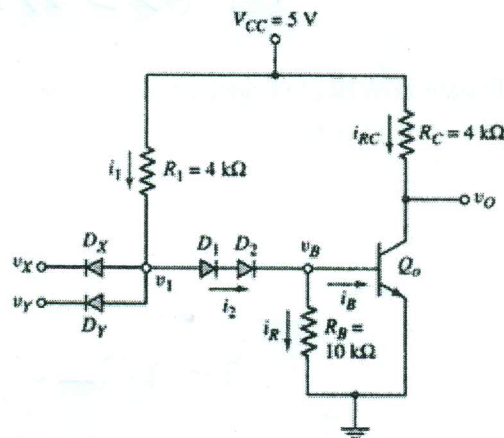


Quiz 2

Name _____

ID: _____

a) Calculate the current i_1 , i_2 , i_R , i_B , i_{RC} . Determine the total power dissipation of the following DTL gate. Given, $V_x = V_y = 5V$ (Logic high) and $V_x = V_y = 0.2V$ (Logic low). Given, $V_{(\text{Diode})on} = 0.7V$; $V_{BE(SAT)} = 0.8V$ and $V_{CE(SAT)} = 0.2V$. [10]



For $V_x = V_y = 5V$;

$$i) \quad v_1 = v_{D1} + v_{D2} + v_{BE(SAT)} = 0.7 + 0.7 + 0.8 = 2.2V$$

$$ii) \quad i_1 = \frac{V_{CC} - v_1}{R_1} = \frac{5 - 2.2}{4} = 0.7mA$$

$$iii) \quad i_2 = i_1 = 0.7mA$$

$$iv) \quad i_R = \frac{v_{BE(SAT)}}{R_B} = \frac{0.8}{10} = 0.08mA$$

$$v) \quad i_B = i_2 - i_R = (0.7 - 0.08) = 0.62mA \quad vi) \quad i_{RC} = \frac{V_{CC} - v_O}{R_C}$$

$$vii) \quad \text{Power}_{high} = V_{CC} (i_1 + i_{RC}) = \frac{5 - 0.2}{4} = 1.2mA$$

$$P_{high} = 9.5mW$$

For $V_x = V_y = 0.2V$; $V_1 = V_{Dx} + V_x = 0.7 + 0.2 = 0.9V$

$$P_{Low} = V_{CC} \times i_1 = V_{CC} \left(\frac{V_{CC} - 0.9}{4} \right) = 5 \times \frac{4.1}{4}$$


Total power = $P_{high} + P_{Low}$, $= 9.5 + 5.125mW$

$$= 14.625mW$$

$$\boxed{\begin{matrix} i_2 = i_P = i_B = \\ i_{RC} = 0 \end{matrix}}$$

b) If output of two DTL NAND gate is WIRED together, what will be the output of the gate?
Draw the circuit diagram and identify the type of logic gate.

[5]

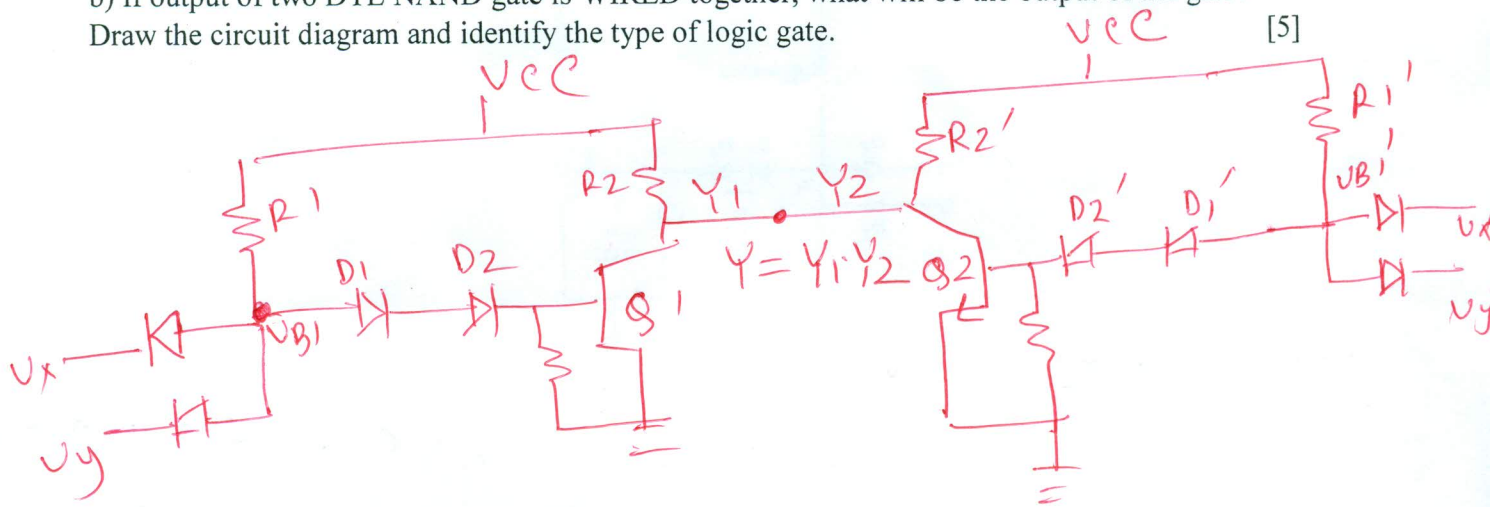

AND gate.

$Y = 1$ if both Y_1 & Y_2 are 1


For all other case $Y = 0$

Quiz 3

Name _____

ID: _____

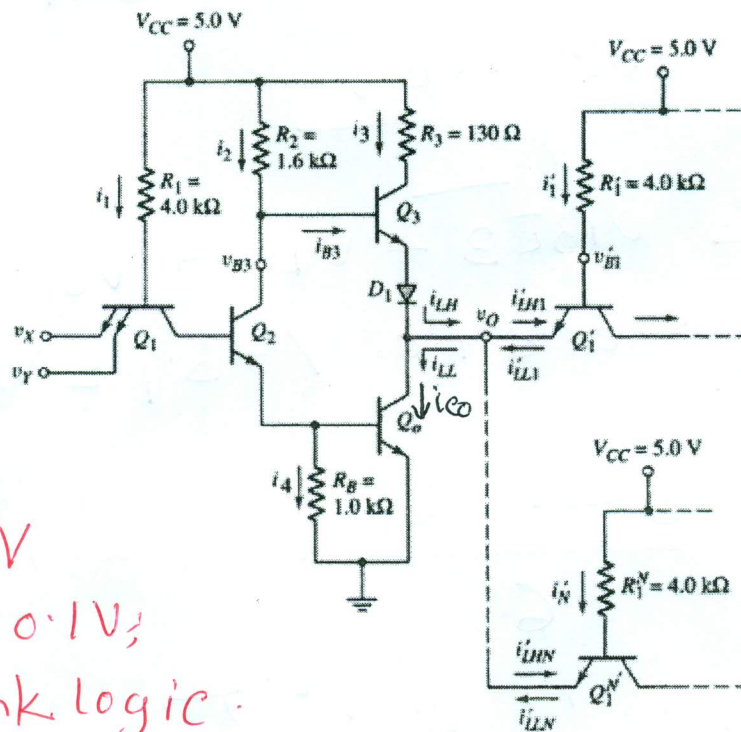1. In the TTL circuit below, the transistors parameters is $\beta = 25$, $\beta_R = 0.2$. Calculate the maximum fan out for (a) $V_X = V_Y = 5V$ and (b) $V_X = V_Y = 0.1V$ and $V_O = 3.1V$. Given rated maximum collector current, $I_{CO(rated)} = 16mA$. $V_{BC(ON)} = 0.7V$, $V_{BE(sat)} = 0.8V$, $V_{CE(sat)} = 0.1V$, $V_{D1(ON)} = 0.7V$. [15]



1) $V_X = V_Y = 5V$

2) $V_O = low = 0.1V$;
current sink logic.

iii) $i_{LH}' = i_{LL}'$

iii) $N \cdot i_{LL}' = i_{CO(rated)}$

$$N = \frac{i_{CO}}{i_{LL}'}$$

$$i_{LL}' = \frac{V_{CC} - V_{B1}'}{R_1'}$$

$$= \frac{5 - (0.8 + 0.1)}{4}$$

$$N = \frac{16}{1.025} \approx 15$$

$$= 1.025mA$$

ii) For $V_X = V_Y = 0.1V$

o/p high, current source logic.

$$1) I_{LH} = I_{E3} = N \cdot I_{LH1}'$$

$$11) \therefore N = \frac{I_{E3}}{I_{LH1}'} = \frac{I_{B3} [1 + \beta \cdot B]}{I_{LH1}'}$$

$$111) I_{B3} = \frac{V_{CC} - V_{B3}}{R_2}$$

$$112) V_{B3} = V_{BE3} + V_{D1} + V_0$$

$$\therefore V_{B3} = 0.8 + 0.7 + 3.1 = 4.6V$$

$$113) I_{B3} = \frac{5 - 4.6}{1.6} = 0.25mA$$

$$114) I_{LH1}' = I_{E1}' = \frac{1}{\beta \cdot R} \cdot i_1'$$

$$i_1' = \left[\frac{V_{CC} - V_{B1}'}{R_{11}} \right] \times 0.2 \quad \text{5 - (0.7 + 0.8 + 0.8)} \quad \text{Q1' R-Active}$$

$$i_1' = \left(\frac{5 - 2.3}{4} \right) \times 0.2 = 0.675 \times 0.2 = 0.135mA$$

$$115) N = \frac{0.25 [1 + (\frac{25 \times 0.85}{21.25})]}{0.135}$$

$$= \frac{0.425}{0.135} \approx 3.15 \approx 3.15 \times 1.35 = 5.56 \approx 41$$