
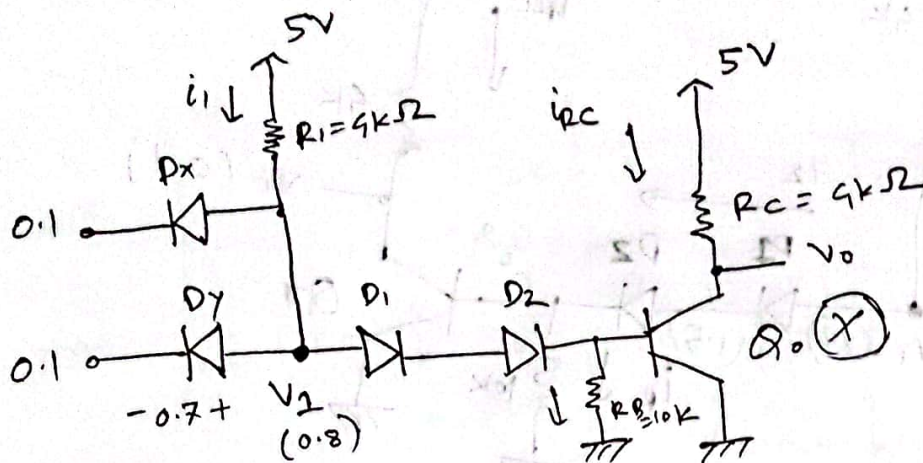


Ans. to the question no. ⁰¹ ~~02~~:

(a)

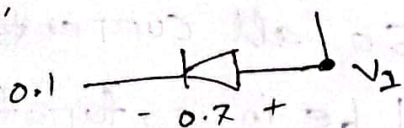

Here,




$V_1 = (0.1 + 0.7) = 0.8V$. This voltage can not turn on the transistor. Therefore, Q_0 will be in cut-off.

$$\therefore i_1 = \frac{5 - 0.8}{9k} = 1.05mA$$

$$\text{And } i_2 = i_R = i_B = i_{RC} = 0$$

(b)

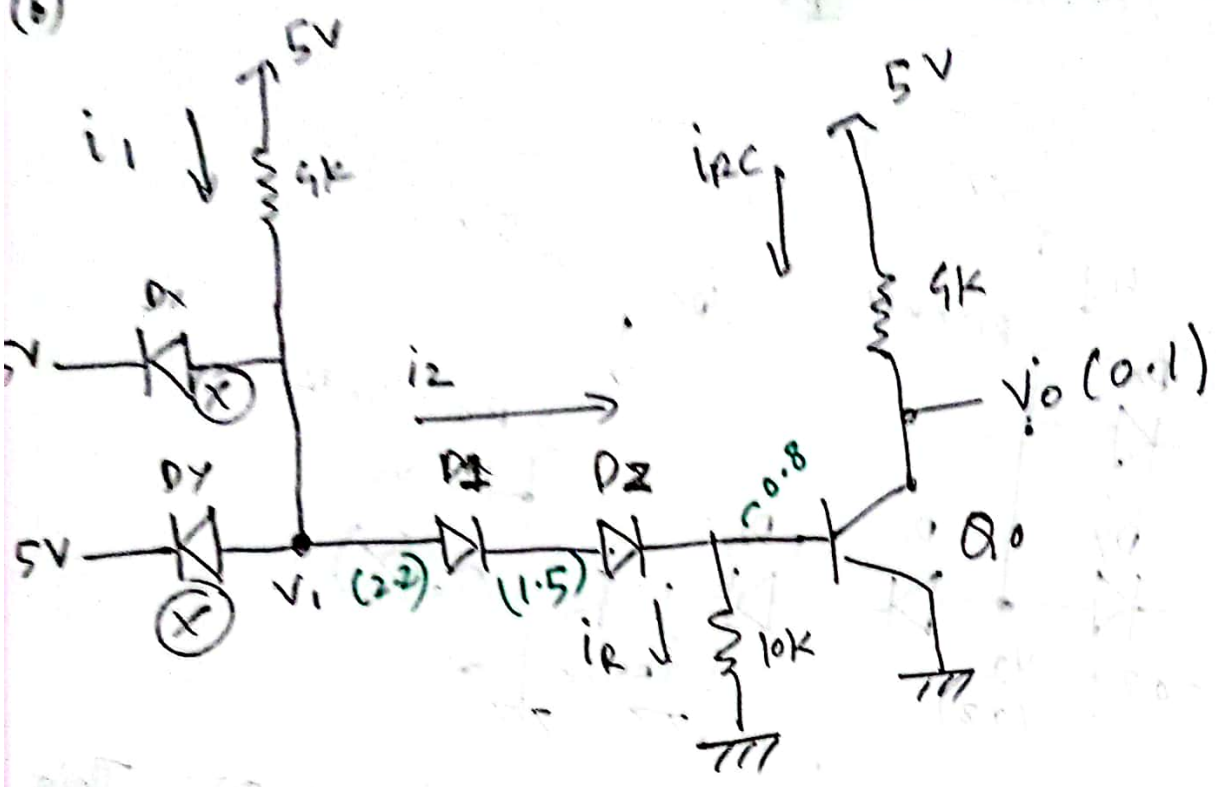

Since, D_x and D_y are off. So all currents will flow through Q_0 , and will be in saturation.

$$\therefore V_0 = V_{CE} = 0.1V \text{ and } V_1 = 2.2V$$

$$\therefore i_1 = \frac{5 - 2.2}{4K} = 0.7mA$$

$$i_2 = i_1 = 0.7mA$$

$$i_R = \frac{0.8 - 0}{10K} = 0.08mA$$


$$\therefore i_2 = i_B + i_R$$

$$\therefore i_B = i_2 - i_R = 0.62mA$$

$$\therefore i_{RC} = \frac{5 - 0.1}{4K} = 1.225mA$$

(Ans)

Ans. to the question no. 02:

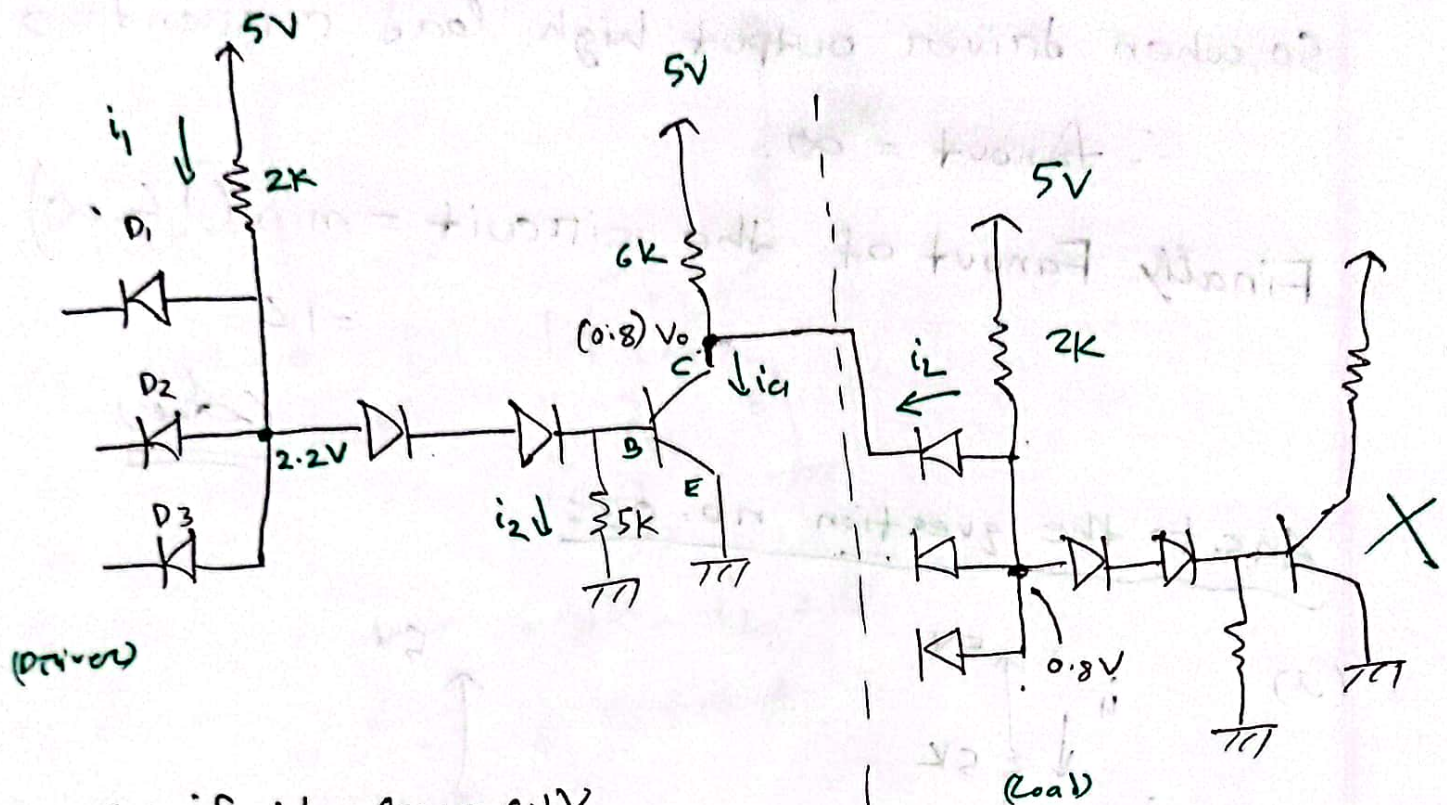

case 1: if $V_0 = \text{low} = 0.1V$

$$i_L = \frac{5 - 0.8}{2k} = 2.1 \text{ mA}$$

$$i_3 = \frac{5 - 0.1}{6k} = 0.817 \text{ mA}$$

$$\text{So, } i_{C'} = i_L \times N + i_3$$

Now,

$$i_L \times N + i_3 = \beta_{forced} \times i_B$$

$$\Rightarrow 2.1 \times N + 0.817 = 25 \times 13$$

$$\Rightarrow 2.1 \times N$$
$$\therefore N = \left[\frac{(25 \times 1.24) - 0.817}{2.1} \right]$$
$$= 14$$

$$i_1 = \frac{5 - 2 \cdot 2}{2k} = 1.4 \text{ mA}$$

$$i_2 = \frac{0.8 - 0}{5k} = 0.16 \text{ mA}$$

$$i_B = i_1 - i_2 = 1.24 \text{ mA}$$

Case 2: if $V_0 = \text{high} = 5V$ so, $i_L = 0$

So, when driven output high load current ≈ 0


$\therefore \text{fanout} = \infty.$

Finally Fanout of the circuit = $\min(16, \infty)$.

$$= 14$$

(Ans:)

Ans. to the question no. 03:

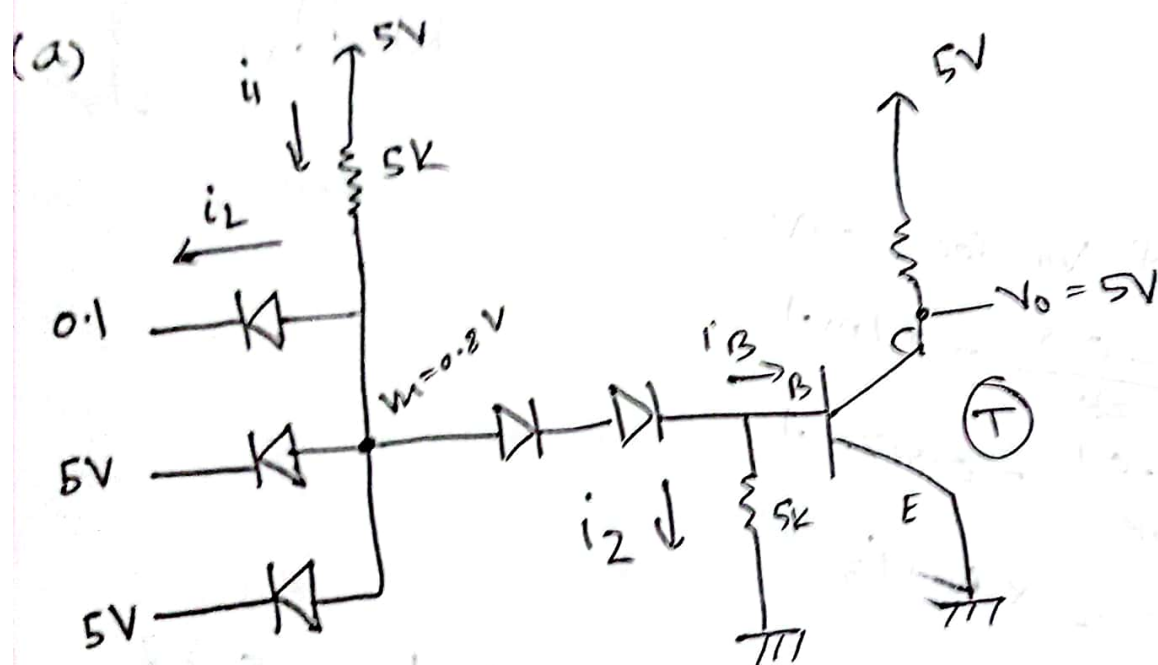


T will be in cut-off.

$$\therefore i_2 = i_B = i_C = 0 \text{ mA}$$

$$\therefore i_1 = i_L = \frac{5 - 0.8}{5k} = 0.84 \text{ mA}$$

(b)

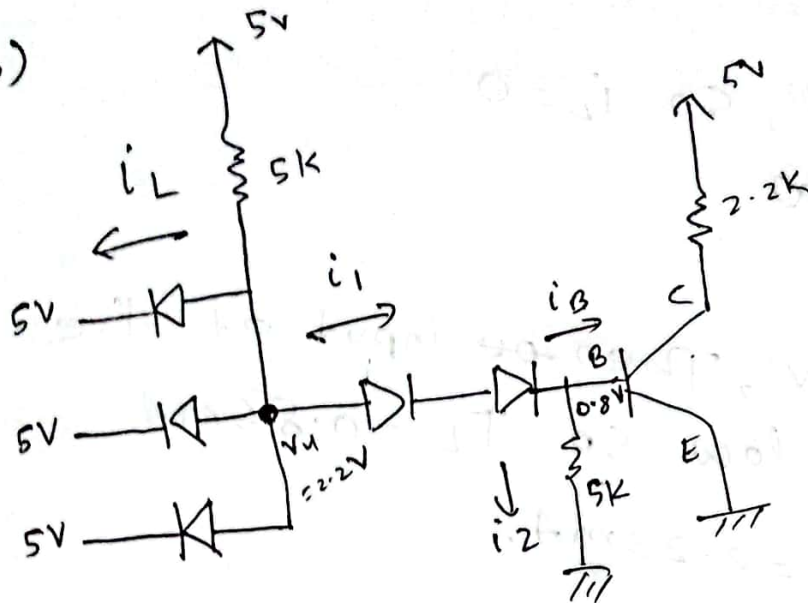

Since inputs are high, $i_2 = 0$

$$\therefore i_1 = \frac{5 - 2.2}{5k} = 0.56 \text{ mA}$$

$$i_2 = \frac{0.8 - 0}{5} = 0.16 \text{ mA}$$

$$i_B = i_1 - i_2 = 0.4 \text{ mA}$$

$$i_C = \frac{5 - 0.1}{2.2k} = 2.23 \text{ mA}$$

c) case 1:

$V_o = \text{high} = 5V$, so $i_L = 0$

$\text{fanout} = \infty$

case 2:

$V_o = \text{low} = 0.1V$, Then ~~the~~ input of the load will be low. so, $I_L = 0.84mA$

$$i_1' = \frac{5 - 0.1}{2.2K} = 2.23mA..$$

$$\therefore i_C = i_1' + i_L \times N$$

$$i_L \times N = 12 - 2.23$$

$$\therefore N = \lfloor 11.63 \rfloor = 11$$

$$\therefore \text{fanout} = \min(\infty, 11)$$

$$= 11 \text{ (Ans.)}$$


(d) Here, inputs are high. Malfunctioning means current will flow the shown direction. To conduct V_A should be

$$(2.2 - 0.6) = 1.6 \text{ V}$$

$$\therefore 5 \text{ V} + N = 1.6 \text{ V}$$

$$\therefore N = [1.6 - 3.4] = -1.8$$

Noise margin 3.4 V

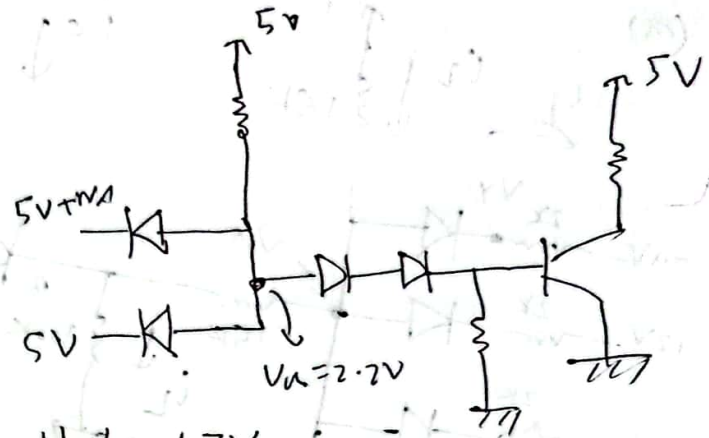

(e) To malfunction V_A should be 1.7 V

$$\therefore V_A + N = 1.7$$

$$\therefore N = 1.7 - 0.8 = 0.9 \text{ V}$$

So, Noise margin $= 0.9 \text{ V}$

(f) maximum power dissipation will happen when inputs are High. Here,

$$i_2 = 0.16 \text{ mA}$$


$$i_3 = 0.4 \text{ mA}$$

$$i_L = 2.23$$


$$\therefore P = P_1 + P_2 + P_3$$

$$= 5 (0.16 + 0.4 + 2.23)$$

$$= 13.95 \text{ mW}$$

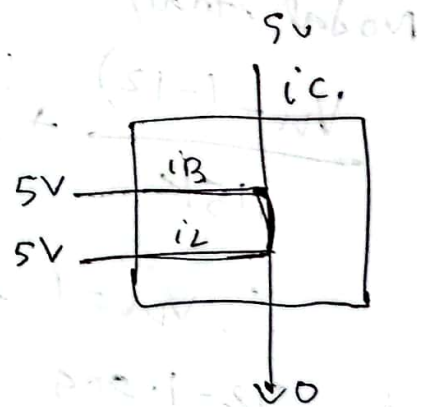

Ans. to the question no. 09:

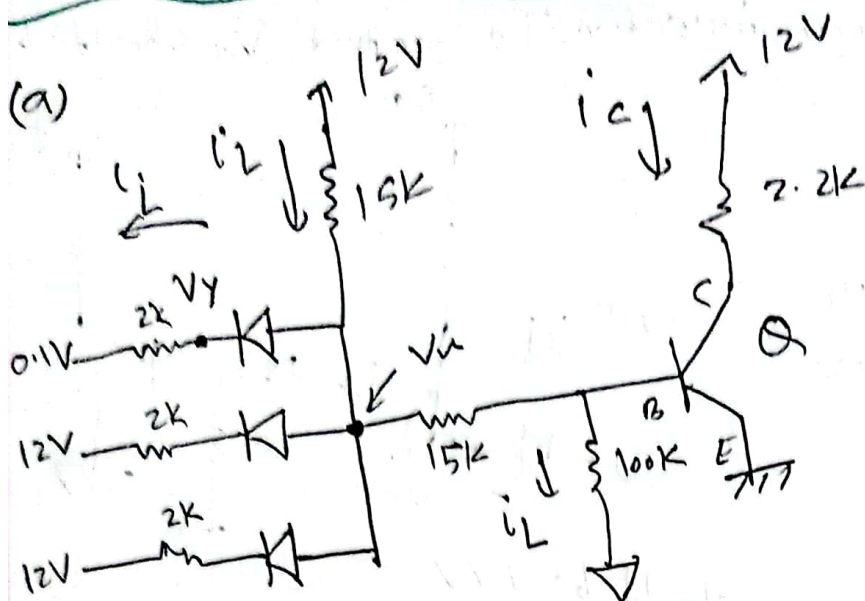

Transistor Q will be in cutoff. So $i_B = i_C = 0 \text{ mA}$

$$\text{Now, } 0.7 \text{ V} = V_u - V_y$$

$$V_y = V_u - 0.7 \text{ V}$$

Nodal Analysis at V_u ,

$$\frac{V_u - (-12)}{115\text{k}} + \frac{(V_u - 0.7) - 0.1}{2\text{k}} + \frac{V_u - 12}{15\text{k}} = 0$$


$$\therefore V_u = 1.904 \text{ V}$$

$$i_1 = \frac{12 - 1.904}{15\text{k}} = 0.673 \text{ mA}$$

$$i_L = \frac{V_u - 0.7 - 0.1}{2\text{k}} = \frac{1.904 - 0.7 - 0.1}{2\text{k}} = 0.552 \text{ mA}$$

$$i_2 = \frac{1.904 + 12}{115} = 0.121 \text{ mA}$$

power dissipation —

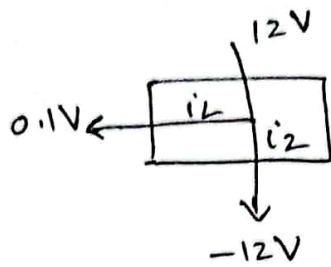

$$\therefore P = i_L (12 - 0.1) + i_2 (12 + 12) = 9.4728 \text{ mW} \quad \underline{\underline{Ans}}$$

(b) Given, $A = B = C = 12 \text{ V}$


$$\therefore i_1 = \frac{12 - 0.8}{30 \text{ k}} = 0.373 \text{ mA}$$

$$i_2 = \frac{0.8 - (-12)}{100 \text{ k}} = 0.128 \text{ mA}$$

$$i_C = \frac{12 - 0.1}{2.2 \text{ k}} = 5.41 \text{ mA}$$

$$i_B = i_1 - i_2 = 0.245 \text{ mA}$$

power dissipation: —

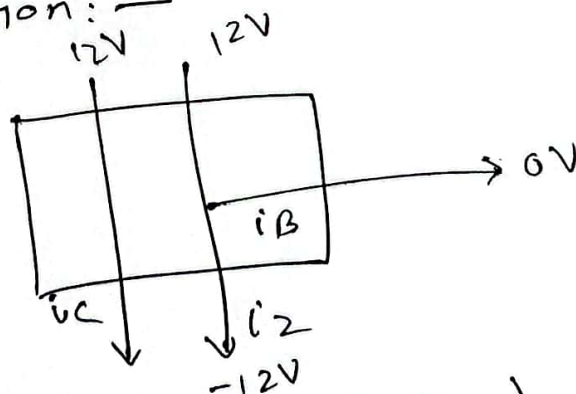

$$\therefore P = i_2 (12 + 12) + i_B (12) + i_C (12)$$

$$= 70.932 \text{ mW} \quad \underline{\underline{Ans}}$$