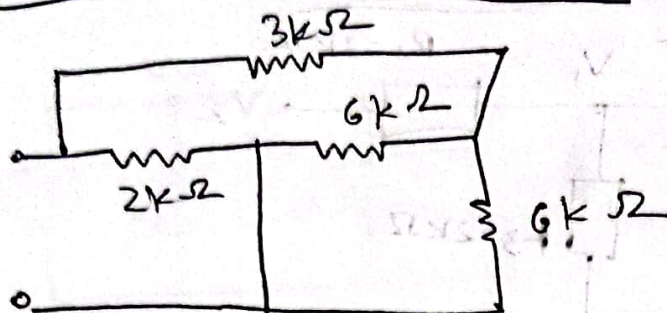


Name: SADAF M. ANIS
ID: 20101537
sec: 11

CSE 350
HW 1

Ans. to the question no. 01:



Here, $6k\Omega$ and another $6k\Omega$ resistor are in parallel.

$$\therefore R_1 = \left(\frac{1}{6} + \frac{1}{6} \right)^{-1} = 3k\Omega$$


Now, R_1 and $3k\Omega$ resistors are in series

$$\therefore R_2 = (3 + 3) = 6k\Omega$$

Finally R_2 and $2k\Omega$ are in parallel.

$$\therefore R_{eq} = \left(\frac{1}{6} + \frac{1}{2} \right)^{-1} = 1.5k\Omega$$

Ans. to the question no. 02:

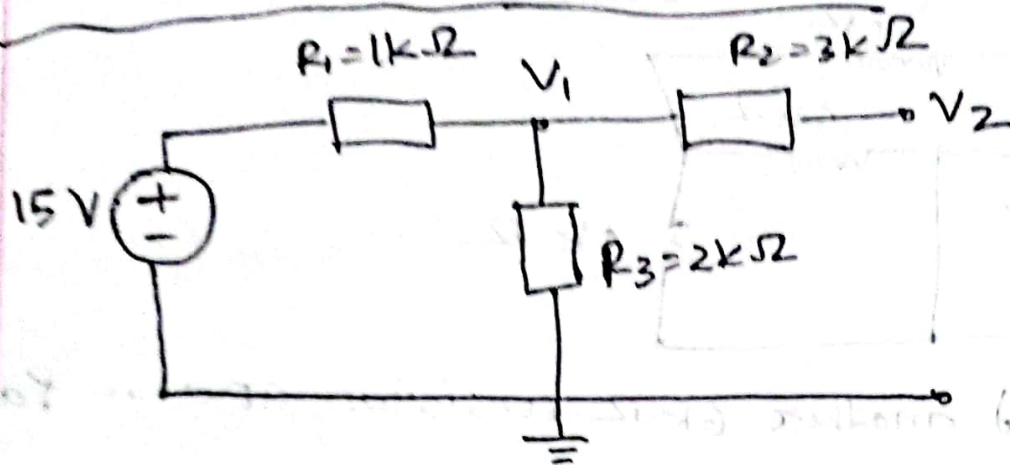

At V_1 -

$$V_1 \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{3} \right) - \frac{15}{1} - \frac{V_2}{3} = 0 \quad \text{--- (I)}$$


Since, no current flow between V_1, V_2 .

$$\text{So, } V_1 = V_2 \quad \text{--- (II)}$$

By calculation, $V_1 = 10V$
 $V_2 = 10V$

Open circuit output is 10V.

Ans. to the question no.03:

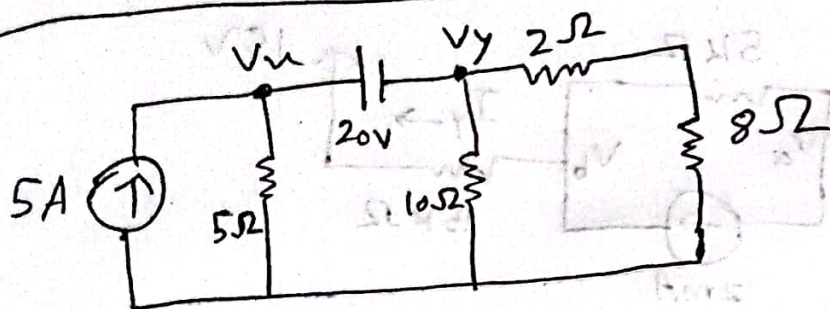

Here, V_x and V_y together \rightarrow supernode.



$$\frac{V_x - 0}{5} - 5 + \frac{V_y - 0}{10} + \frac{V_y - 0}{2+8} = 0 \quad \text{--- (I)}$$

$$\text{Again, } V_x - V_y = 20 \quad \text{--- (II)}$$


By calculating, $V_x = 22.5\text{V}$, $V_y = 2.5\text{V}$

\therefore voltage across the current source, $(V_x - 0) = 22.5\text{V}$ (Ans)

Ans. to the question no.04:

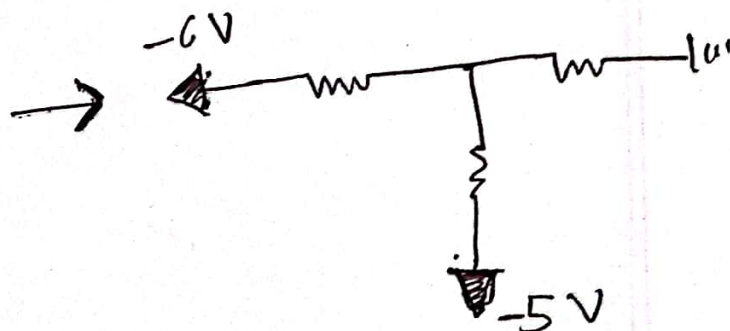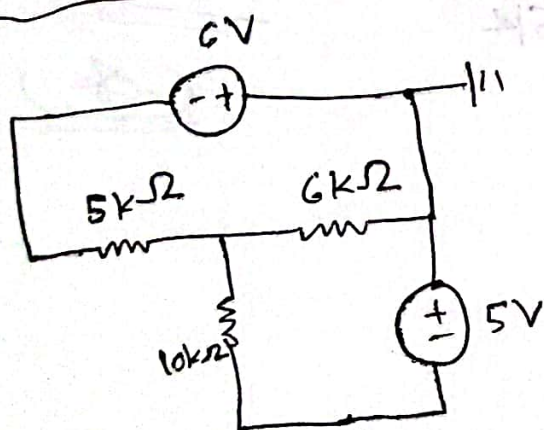

Ans. to the question no. 05

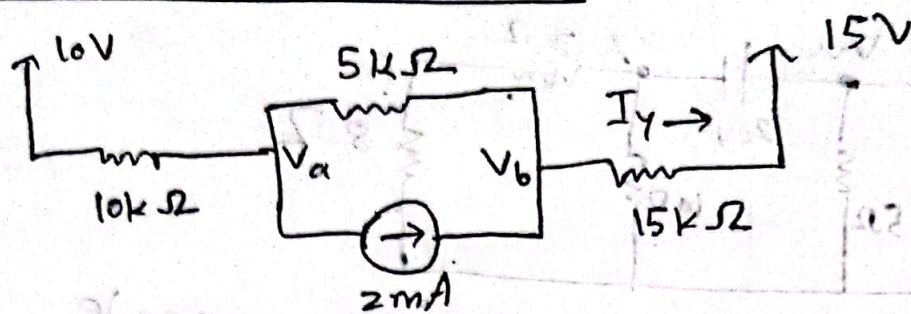

For node V_a -

$$\frac{V_a - 10}{10k} + 2mA + \frac{V_a - V_b}{5k} = 0 \quad \text{--- (i)}$$

For node V_b -

$$\frac{V_b - V_a}{5k} - 2mA + \frac{V_b - 15}{15k} = 0 \quad \text{--- (ii)}$$

By calculating $V_a = 8.33V$
 $V_b = 17.5V$

$$\therefore I_y = \frac{V_b - 15}{15k} = \frac{17.5 - 15}{15k} = \underline{\underline{0.167mA}}$$

